

## CDS1114 Introduction to Digital Systems

### Tutorial 3

#### Tutorial outcomes

By the end of today's tutorial, you should be able to

- describe the operations of basic logic gates – AND, OR, NOT, XOR, NAND
- recognize the different logic symbols of each gate
- construct timing diagrams for input and output signals for various logic gates


#### Theory based questions

Draw the logic symbol and construct the truth tables and timing diagrams for the following gates showing all possible input combinations


1. 1-input inverter
2. 4-input (quad-input) AND gate
3. 4-input OR gate
4. 4-input NAND gate
5. 4-input NOR gate
6. 3-input (tri-input) XOR gate
7. 3-input XNOR gate
8. 4-input XOR gate
9. 4-input XNOR gate
10. 3-input negative-AND gate
11. 3-input negative-OR gate

#### Applied knowledge questions

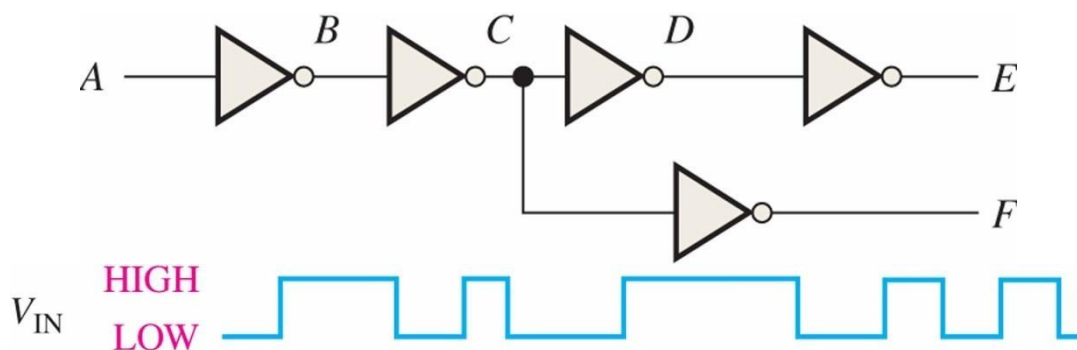
1. A series of *cascaded* inverters is shown in the figure below. Determine the logic level outputs at B, C, D and F if the  $V_{in}$  signal at A is given as shown.



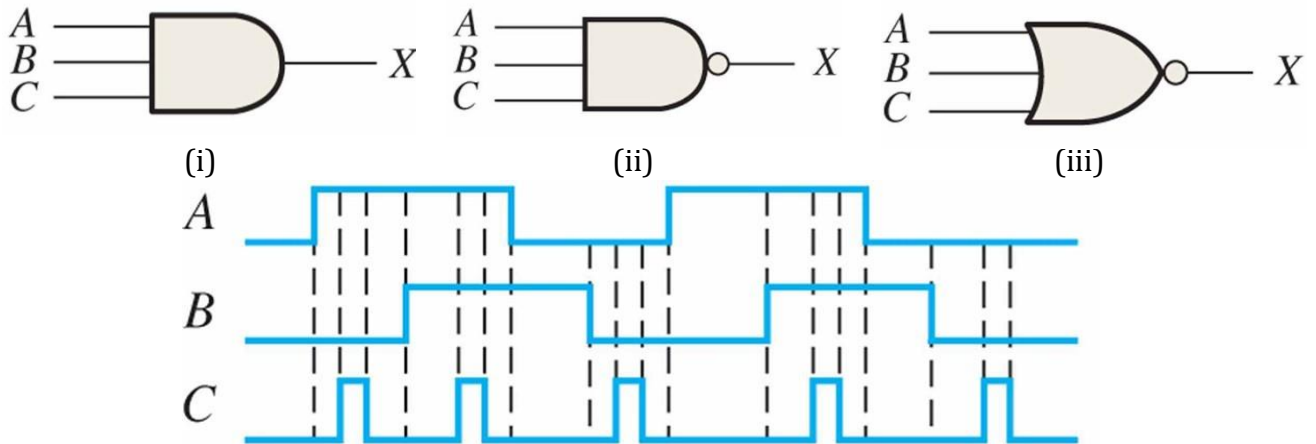
2. Determine the individual outputs of X to the tri-input gates below based on the timing diagrams shown for inputs A, B and C



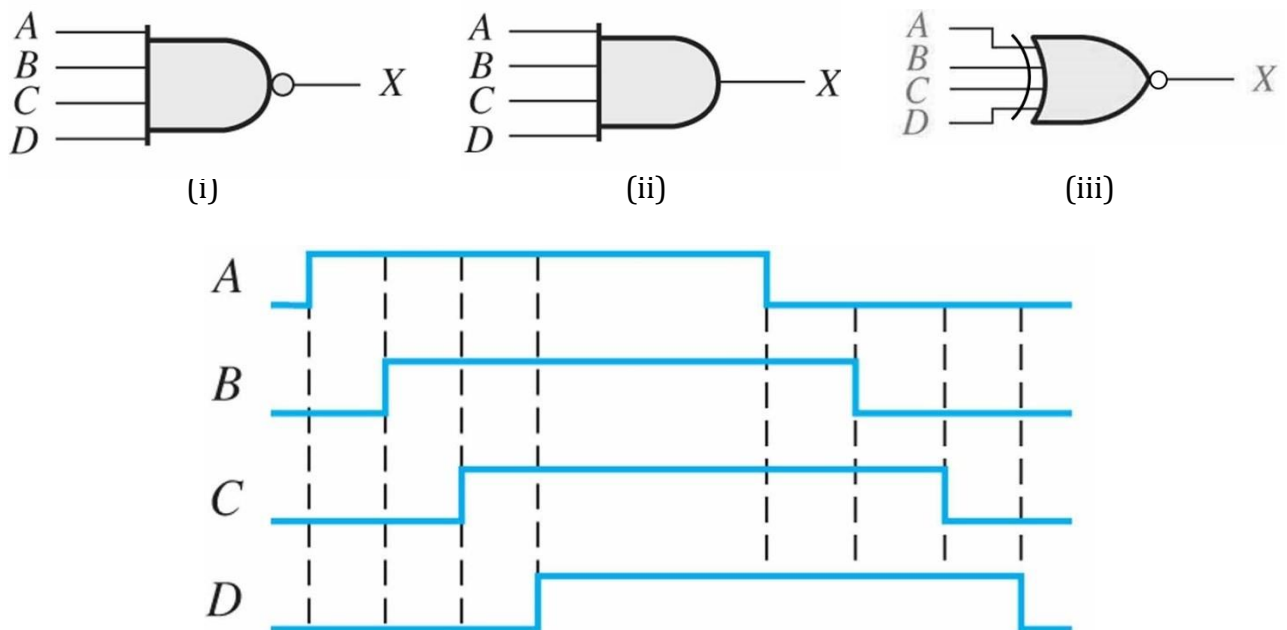3. Determine the individual outputs of X to the quad-input gates below based on the timing diagrams shown for inputs A, B, C and D



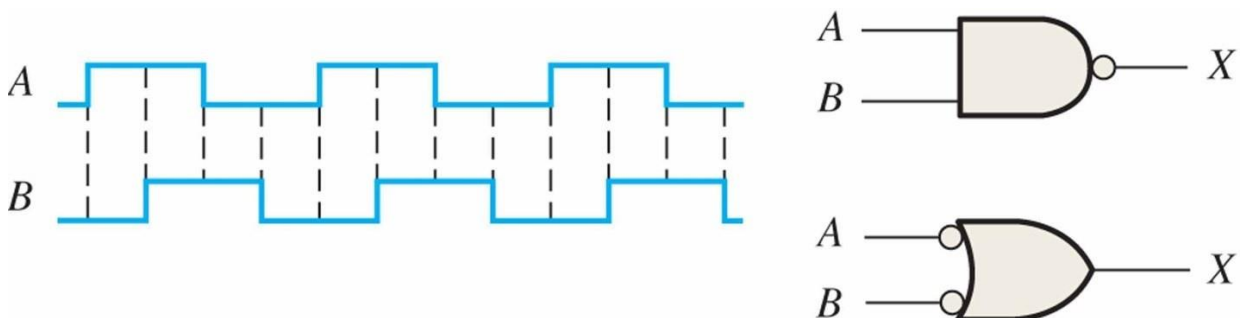4. Complete the timing diagram for the two gates below based on the inputs A and B shown. What conclusions can you derive from the output of the gates?



5. The headlights of a car only turn on (light up) when the car's ignition is turned ON with the key and the headlight switch is turned ON. Assuming that the headlight requires a LOW signal to turn it ON, what gate would be suitable to fit in the blank below to complete the circuit? Explain your answer.

